



Rysunek 1: Schemat układu filtra dolnoprzepustowego

	Obliczone	Zmierzone
C_1 [F]		
C_2 [F]		
R_g [Ω]		
R_1 [Ω]		
R_2 [Ω]		
R_3 [Ω]		
R_4 [Ω]		

Tabela 1: Obliczone i rzeczywiste wartości elementów filtra

	U_{we}	U_{wy}
1		
2		
3		
4		
5		
6		
7		
8		
9		
10		
11		
12		
13		
14		
15		
16		
17		
18		
19		
20		
21		
22		
23		
24		
25		
26		
27		
28		
29		
30		

Tabela 2: Pomiar Charakterystyki $U_{wy} = f(U_{we})$

	f	U_{wy}
1		
2		
3		
4		
5		
6		
7		
8		
9		
10		
11		
12		
13		
14		
15		
16		
17		
18		
19		
20		
21		
22		
23		
24		
25		
26		
27		
28		
29		
30		

Tabela 3: Pomiar Charakterystyki $U_{wy} = f(U_{we})$

